



# Introduction

**Linear Circuit Analysis**

**EECE 202**



***Number of credits: 3 credits***

***Prerequisites: EECE 201***

***Contact Hours: 3 hrs Lecture***

***Textbook/material required:*** R. A. DeCarlo and P-M. Lin, “Linear Circuit Analysis; The Time Domain, Phasor and Laplace Transform Approach”, 3rd Edition, 2009.

## Learning Outcomes

***By the end of this course, the student should be able to:***


- 1. An ability to compute impedances and admittances of components and circuits. SO[1]*
- 2. An ability to compute responses of linear circuits with and without initial conditions via one-sided Laplace transform techniques. SO[1]*
- 3. An ability to compute responses to linear circuits using transfer function and convolution techniques. SO[1]*
- 4. An ability to analyze and compute responses of linear circuits containing mutually coupled inductors and ideal transformers in the s-domain. SO[1]*
- 5. An ability to analyze basic two port circuits using the various types of two port parameters and be able to construct such parameters from a given circuit. SO[1]*
- 6. An ability to analyze and design basic LP, BP, HP and resonant circuits in the s-domain. SO[1]*
- 7. an ability to work within a team, develop hands-on experience, draw conclusion and communicate results through the offered course project. SO[2,3,5]*

	Assessment		Weight
Attendance			5%
Assignments	PD1 – Conceptual Design Presentation (Week 10)		3 x 10%
	PD2 – Technical Report (10%) (Week 12)		
	PD3 – Prototype Demonstration (10%) (Week 14)		
Graded Class Activity (GCA)	GCA – 1 (Week 6, L2)		2 x 10%
	GCA – 2 (Week 11, L2)		
Moodle Quiz	Quiz (Week 4)		5%
Midterm	Week 8		20%
Final exam	Week 16		20%
		Total	100%




# Revision on EE201


# Passive Elements

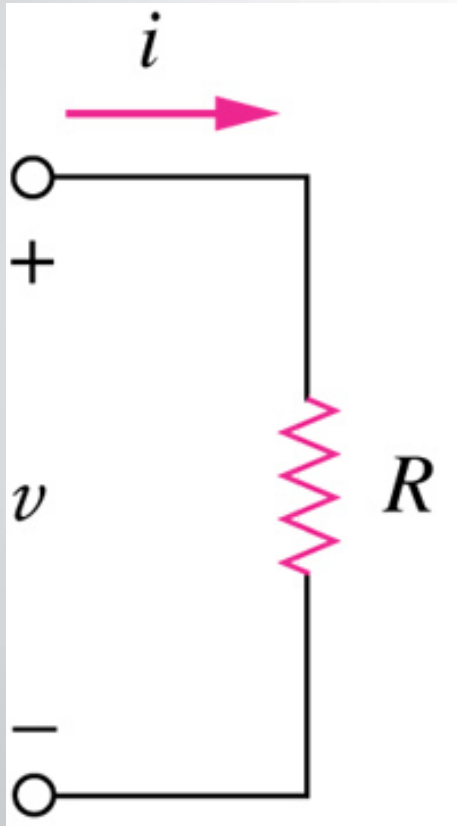

**Resistor**

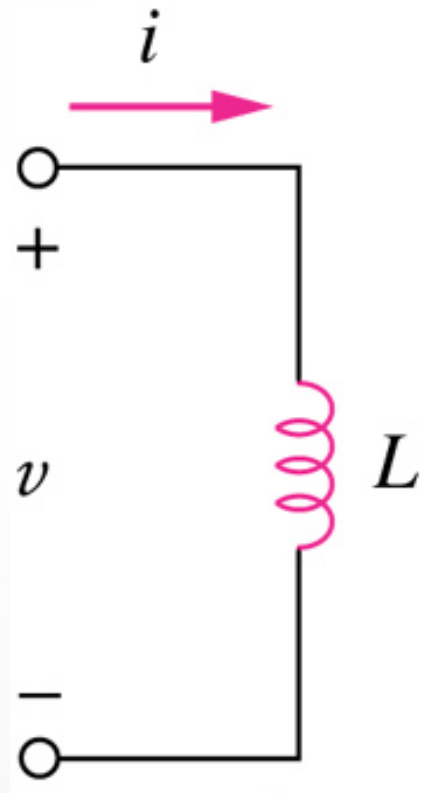


**Inductor**

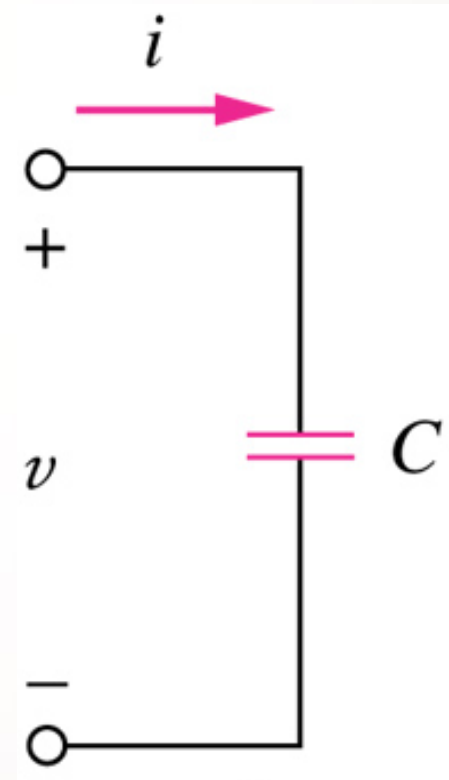

**Capacitor**

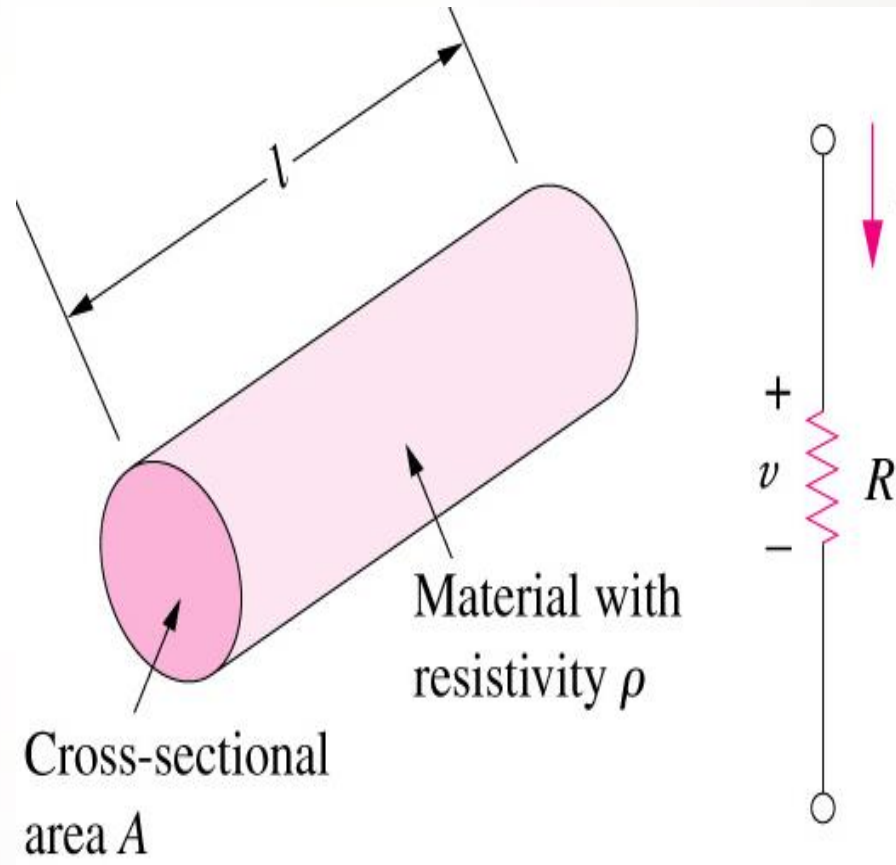
# Ohm's Law

*Ohm's law states that the voltage "V" across a resistor "R" is directly proportional to the current "I" flowing through the resistor*




$$V = I \times R$$

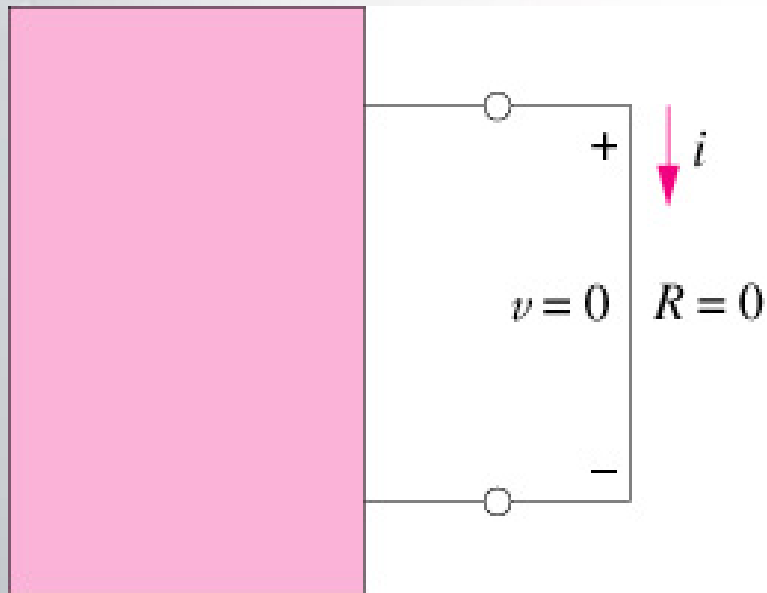As  $R$  varies from **zero** to **infinity**, it is necessary to study the relation between  $V$  and  $I$  at the extreme values of  $R$



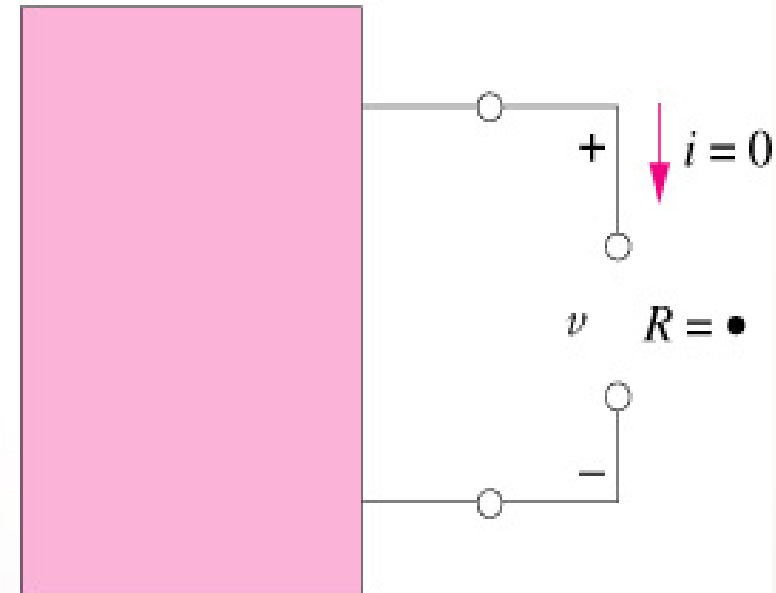
Short Circuit Case  
 $R = \text{zero}, V = \text{zero}$



Open Circuit Case  
 $R = \infty, I = \text{zero}$


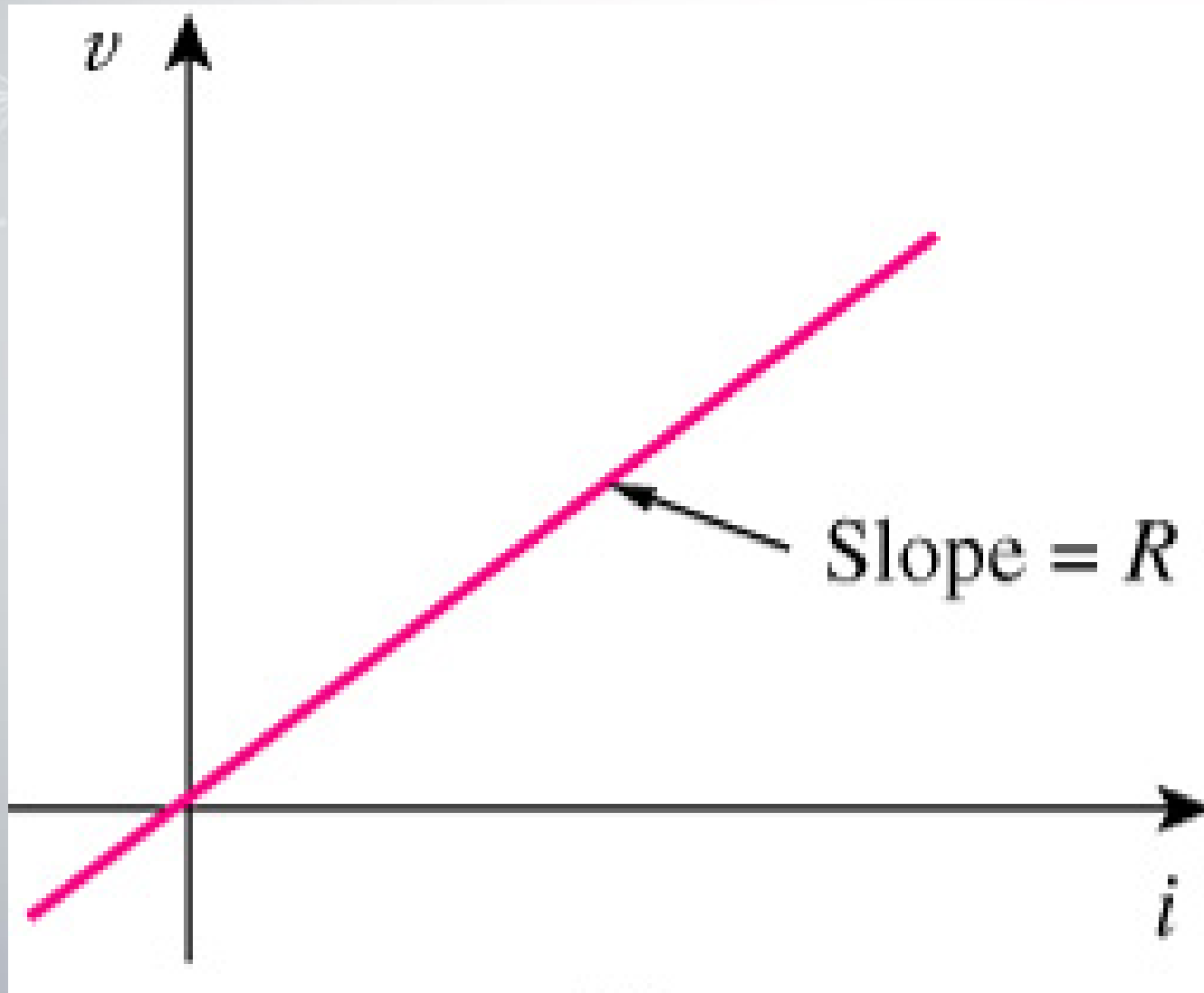
# V-I characteristics according to Ohm's law




$$V = I \times R$$

$$I = V/R$$

$$R = V/I$$

# Power calculations according to Ohm's Law

$$V = I \times R$$

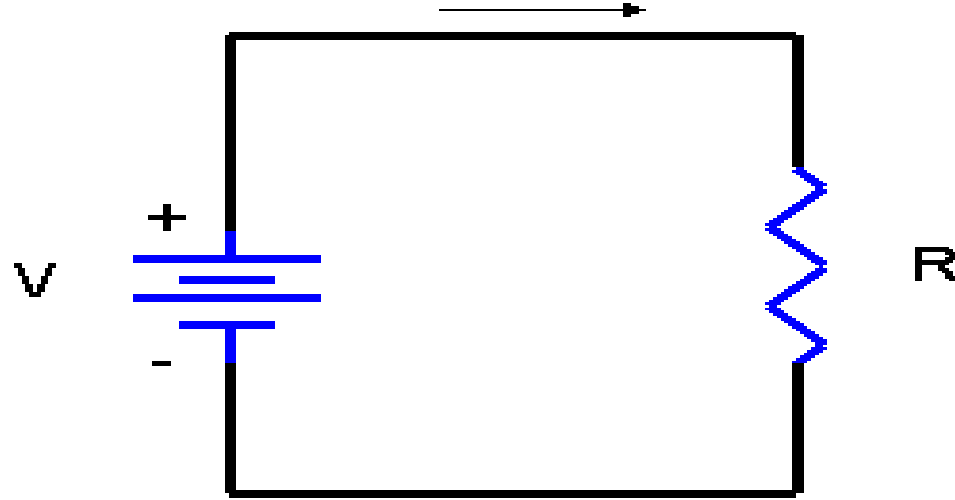

$$P = I^2 \times R$$


$$P = V \times I$$

$$P = V^2 / R$$

# Ohm's law

P = Power

I = Current

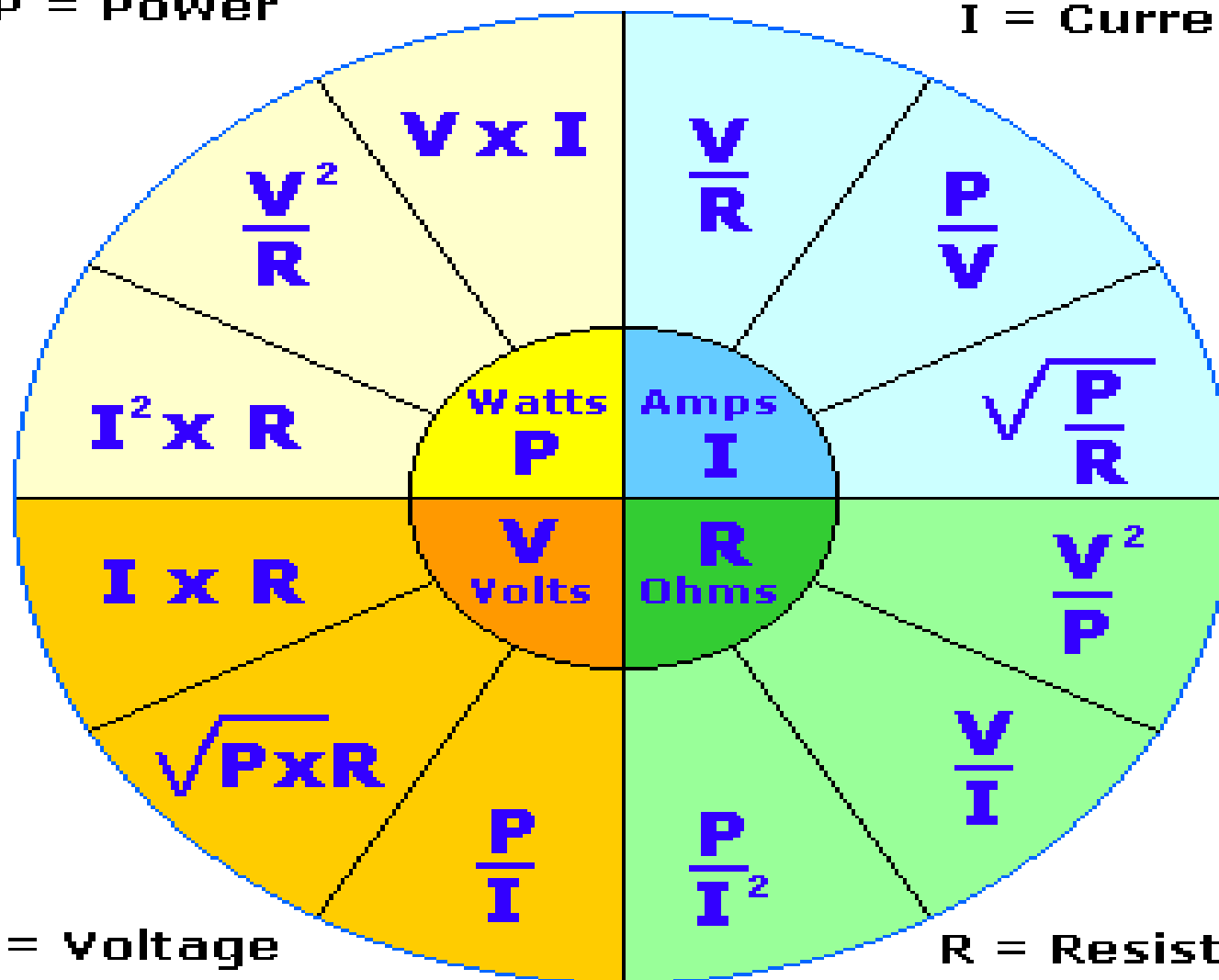

V = Voltage

R = Resistance

## Example 7

A resistor formed of a copper conductor of length 0.1 m and cross-sectional area  $4 \times 10^{-4} \text{ m}^2$ , the resistivity of copper is  $1.72 \times 10^{-8} \Omega \cdot \text{m}$  find the current flowing through the resistor when a 10 V battery is connected across its terminals.

### Solution


$$\text{Since } I = V/R$$

$$\text{And } R = \rho L/A = 1.72 \times 10^{-8} \times 0.1 / 4 \times 10^{-4} = 43 \times 10^{-7} \Omega$$

$$\text{Then } I = 10 / 43 \times 10^{-7} = 2.3 \text{ MA}$$
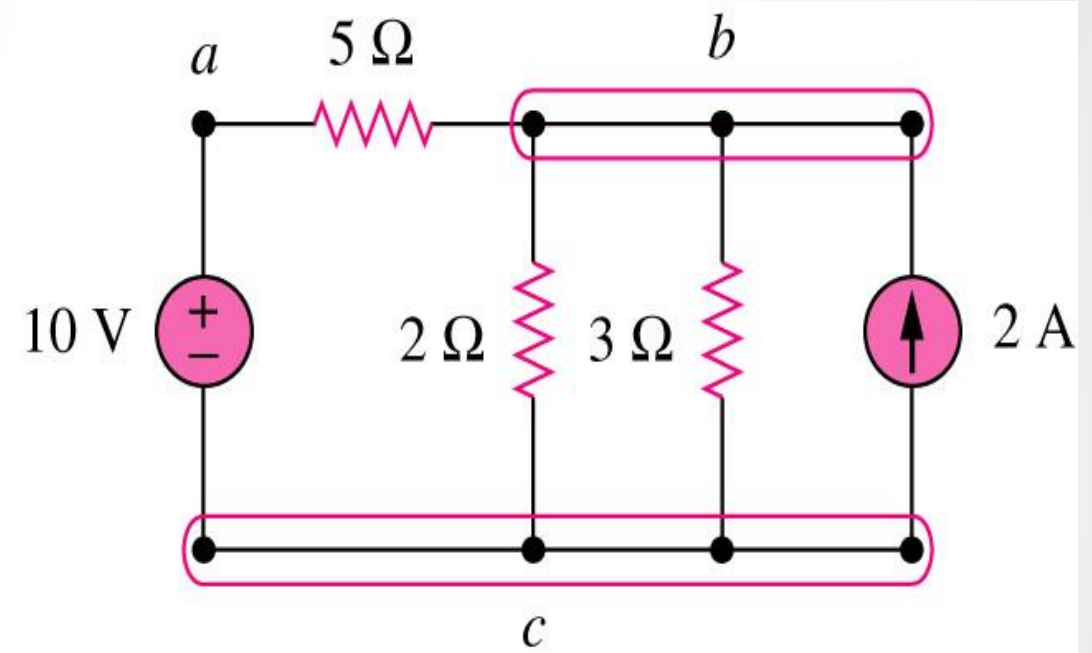
# Nodes, Branches and Loops

**Branch:** represents a single element such as a voltage source or a resistor



*A branch represents any element with two terminals*


$$(V_b - 10)/5 - (V_b/2) - (V_b/3) - 2 = 0$$

There are five branches in the shown figure, namely the 10 V voltage source, the 2-A current source and the three resistors.
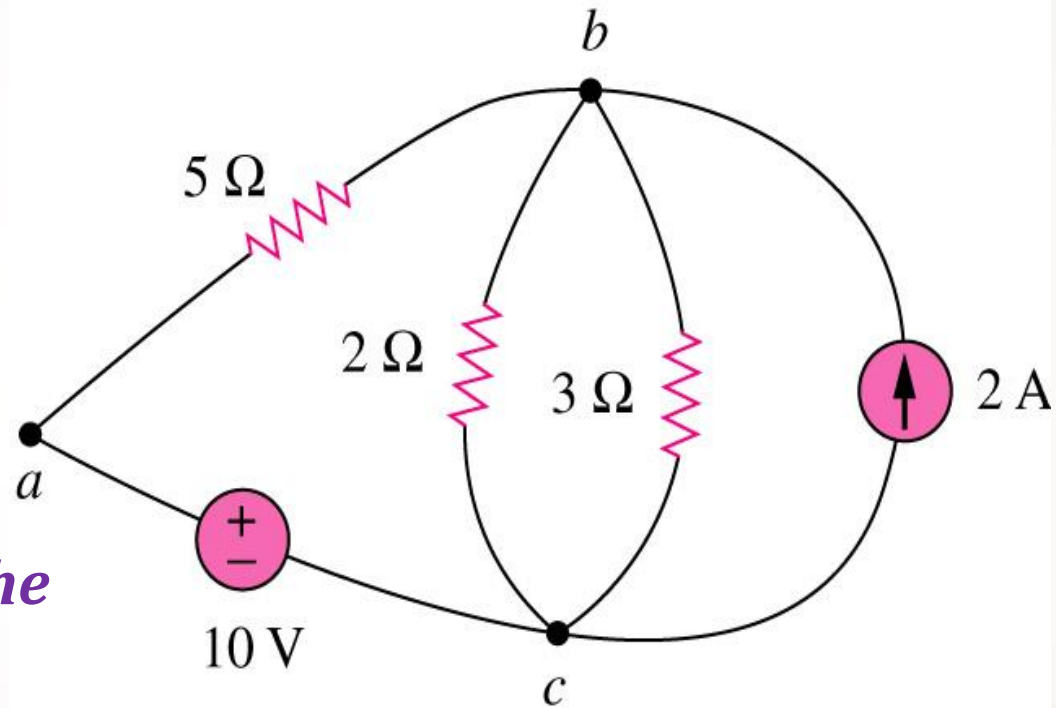
# Nodes, Branches and Loops

**Node:** is the point of connection between two or more branches


*There are three nodes in the shown circuit,  $a$ ,  $b$  and  $c$*



A node is usually indicated by a dot in a circuit, but if a short circuit connects two nodes, the two nodes constitute a single node
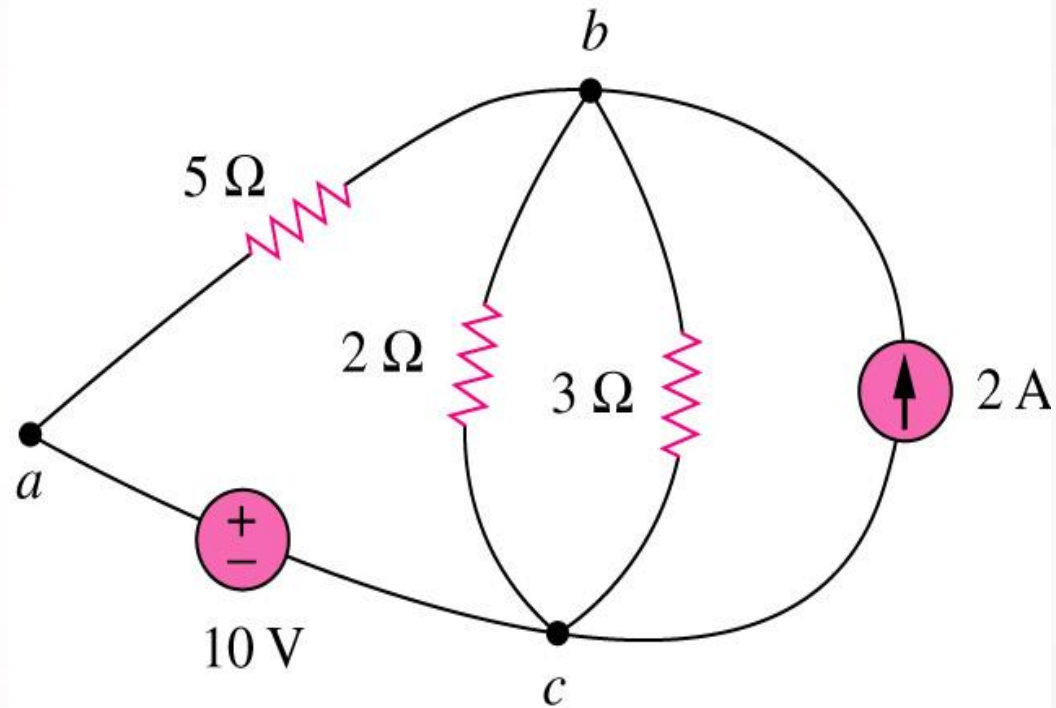
# Nodes, Branches and Loops


**Loop:** is a closed path formed by starting at a node, passing through a set of nodes and returning to the starting node without passing through any node more than once



*abca is a loop, where the flow from b to c could be done via: the 2 ohm resistor, the 3 ohm resistor, .....etc*
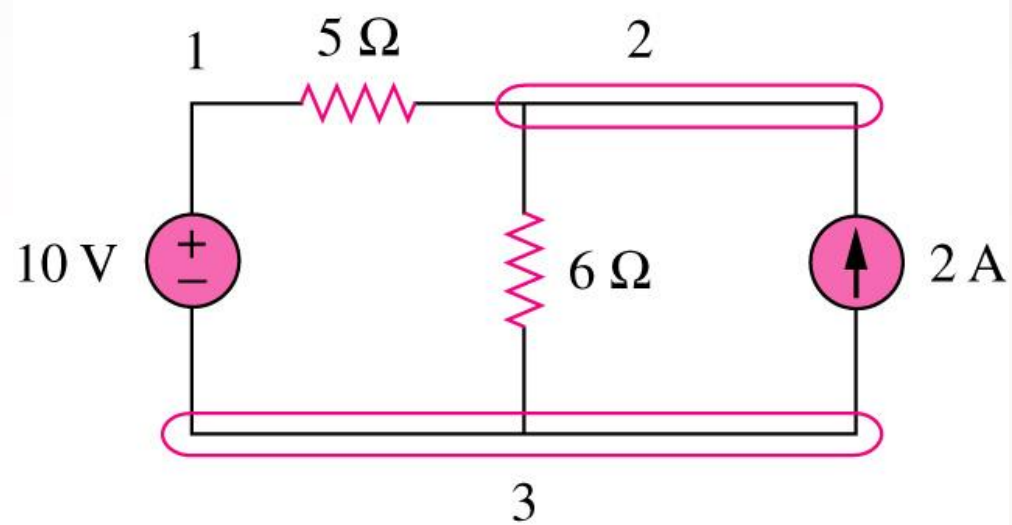
## Example(8)

Determine the number of branches and nodes in the shown circuit



### Solution

As the circuit has four elements, then there are *four branches* as follows:

- ❑ the 10 V voltage source
- ❑ the 2A current source
- ❑ the 5 ohm resistor
- ❑ the 6 ohm resistor


$$(V_2 - 10/5) + (V_2/6) - 2 = 0$$

There are *three nodes* in the circuit 1, 2 and 3


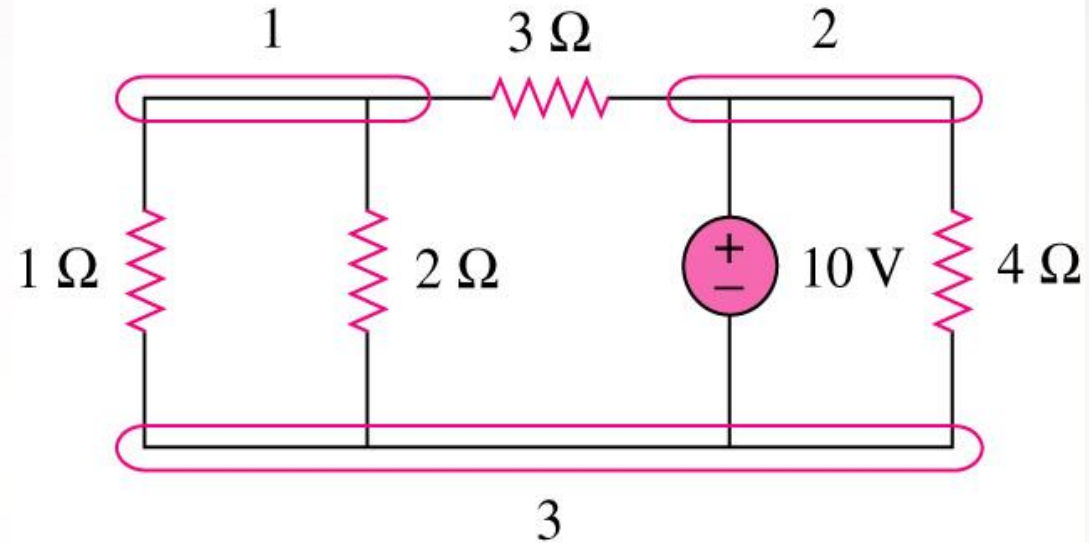
## Example(9)

Determine the number of branches and nodes in the shown circuit



## Solution

As the circuit has five elements, then there are *five branches* as follows:

- ☐ the 10 V voltage source
- ☐ the 1ohm resistor
- ☐ the 2 ohm resistor
- ☐ the 3 ohm resistor
- ☐ the 4 ohm resistor

There are *three nodes* in the circuit 1, 2 and 3

# Resistor's Arrangements

*There are three possible arrangements for resistors in an electrical circuit*



**Series**



**Parallel**



**Series  
&  
Parallel**

# Resistors in Series




Two or more elements are said to be in series if they exclusively share a single node and consequently carry the same current

$$V = V_1 + V_2 = I R_1 + I R_2 = I (R_1 + R_2)$$

$$V = I R_{eq}$$

For N resistors placed in series

$$R_{eq} = R_1 + R_2 + \dots R_N$$

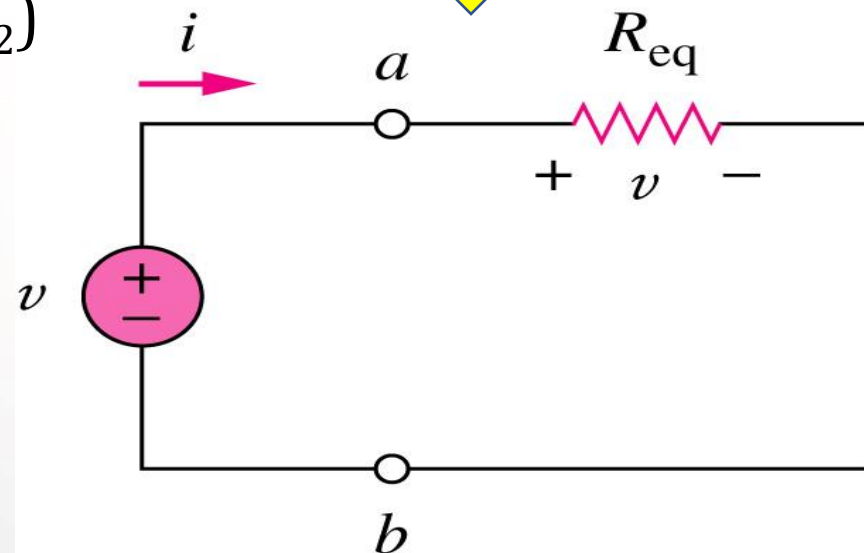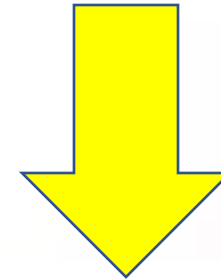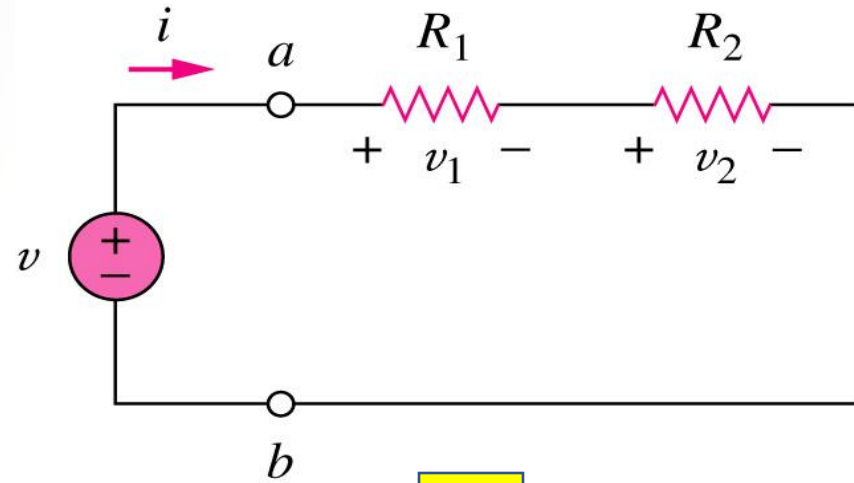

# Resistors in Parallel

Two or more elements are said to be in parallel if they are connected to the same two nodes and consequently have the same voltage across them

$$V = I_1 R_1 = I_2 R_2$$

But since  $I = I_1 + I_2$ , then


$$I = (V/R_1 + V/R_2) = V (R_1 + R_2) / R_1 R_2$$

and as,  $R_{eq} = V/I$ ...then

$$R_{eq} = R_1 R_2 / (R_1 + R_2)$$

For N resistors placed in parallel
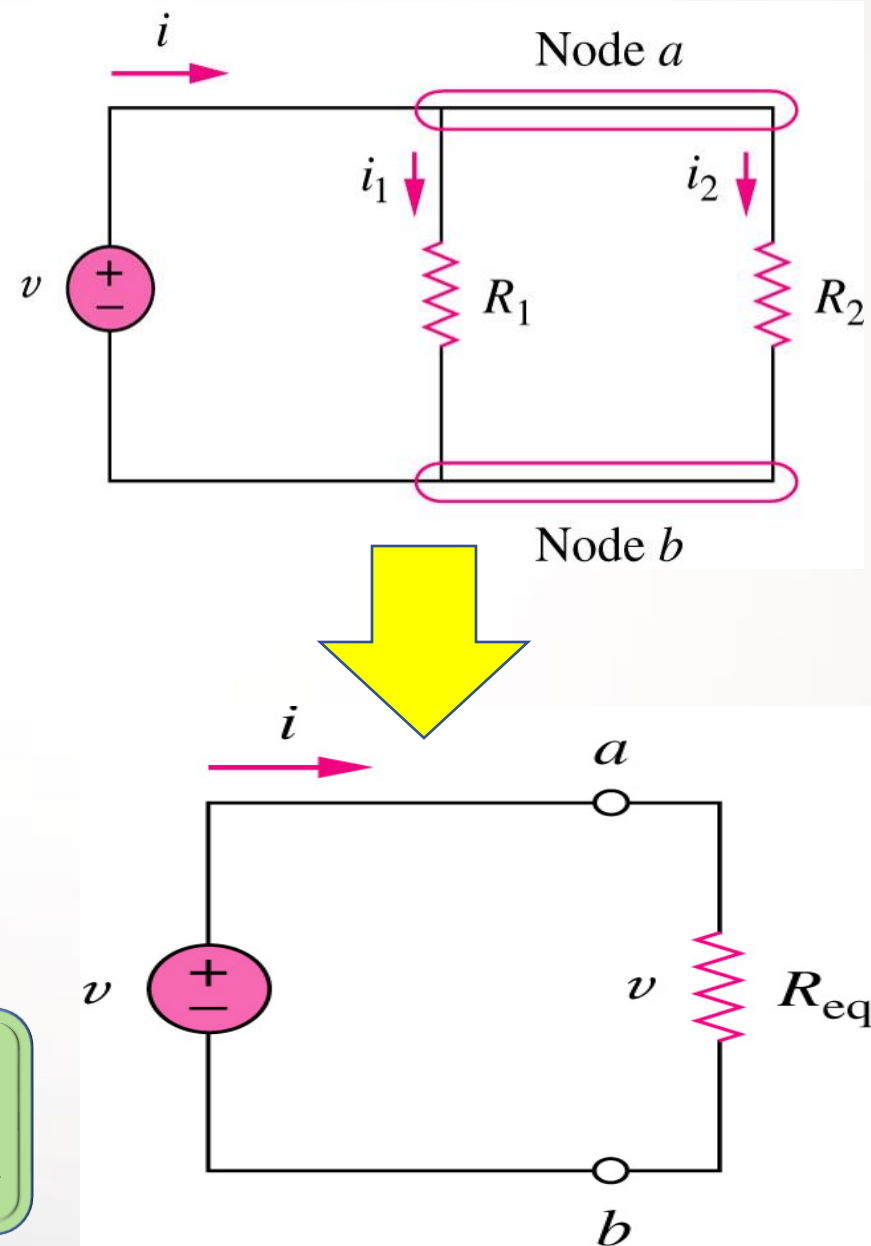
$$1/R_{eq} = 1/R_1 + 1/R_2 + \dots + 1/R_N$$



# Conductance “G”

The conductance is a measure of how well an element will conduct electric current


The unit of conductance is “Siemens” and with the symbol of “S”

$$G = 1/R = I/V \text{ (S)}$$

Note: the equivalent of N parallel resistors could be calculated using conductance, where:

$$G_{eq} = G_1 + G_2 + \dots G_N$$

# Voltage sources placed in Series


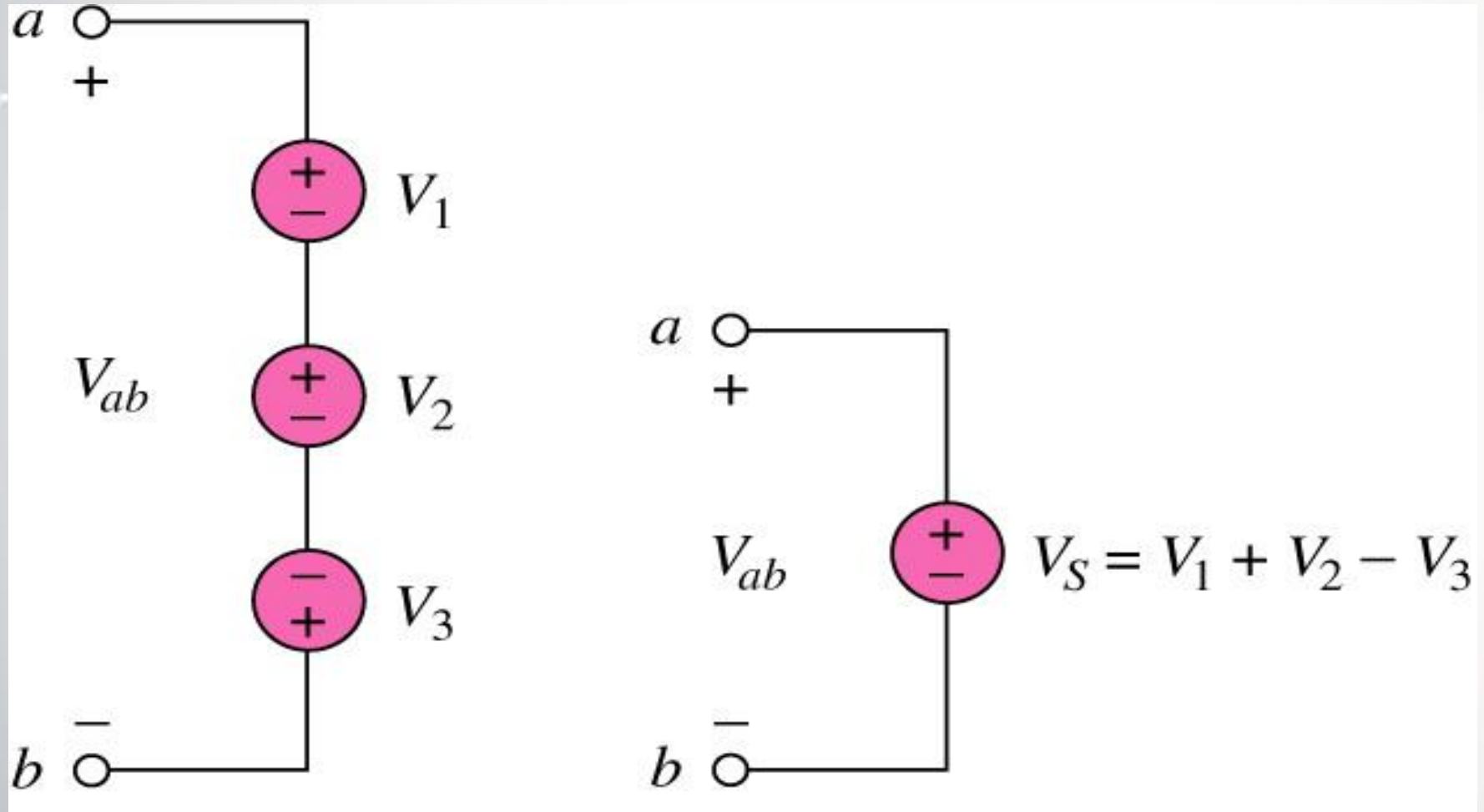


*Note the voltage source sign when obtaining their equivalence*

## Example(10)

Find  $R_{eq}$  for the shown resistor arrangement

**Solution**

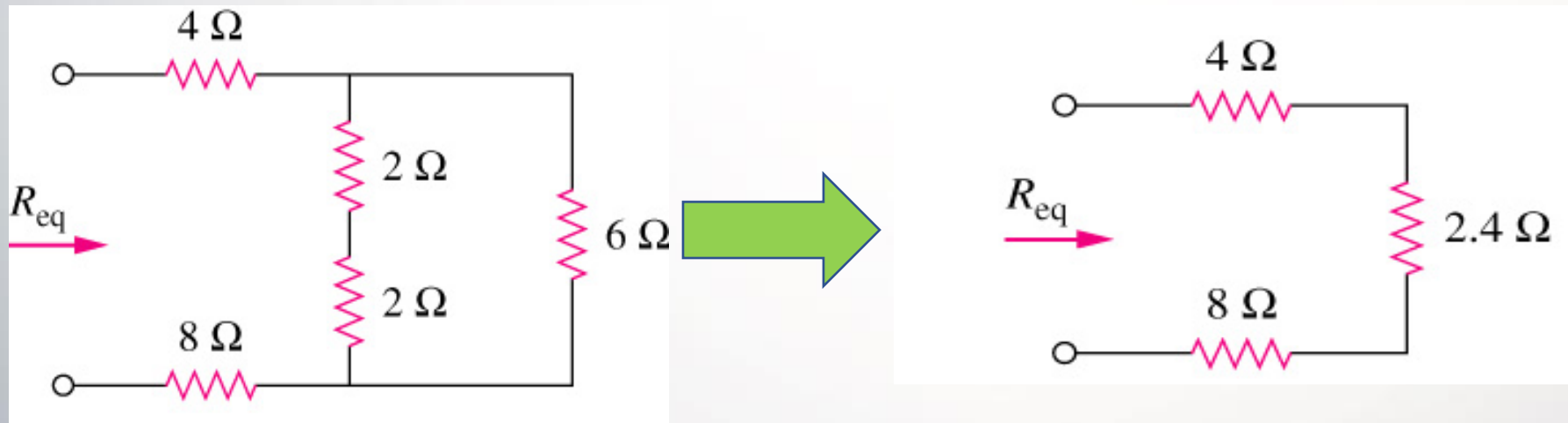
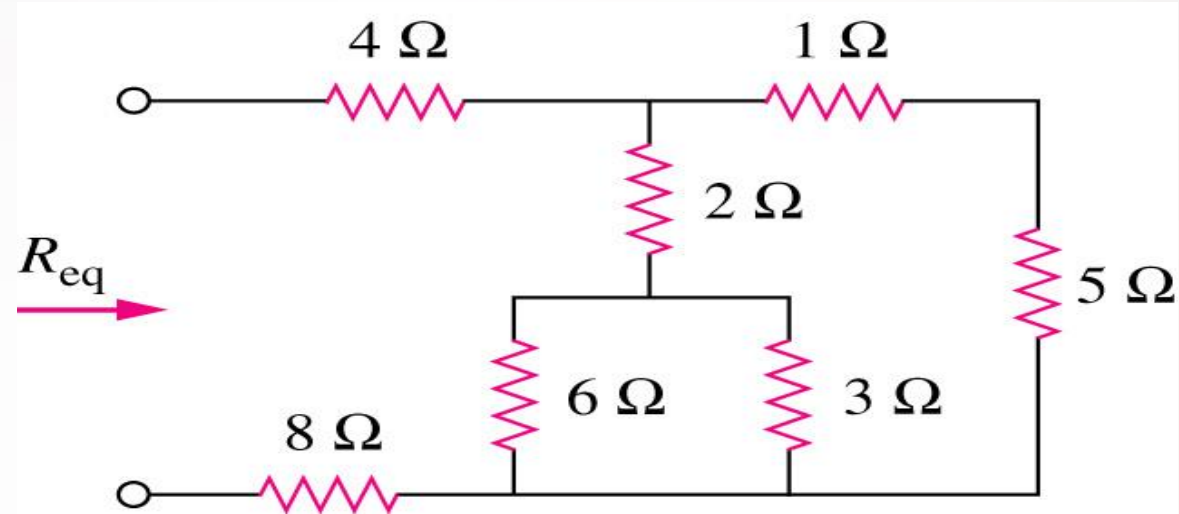


$$R_{eq} = 4 + 8 + 2.4 = 14.4\ \Omega$$

## Example(11)

Find  $R_{eq}$  for the shown resistor arrangement

**Solution**

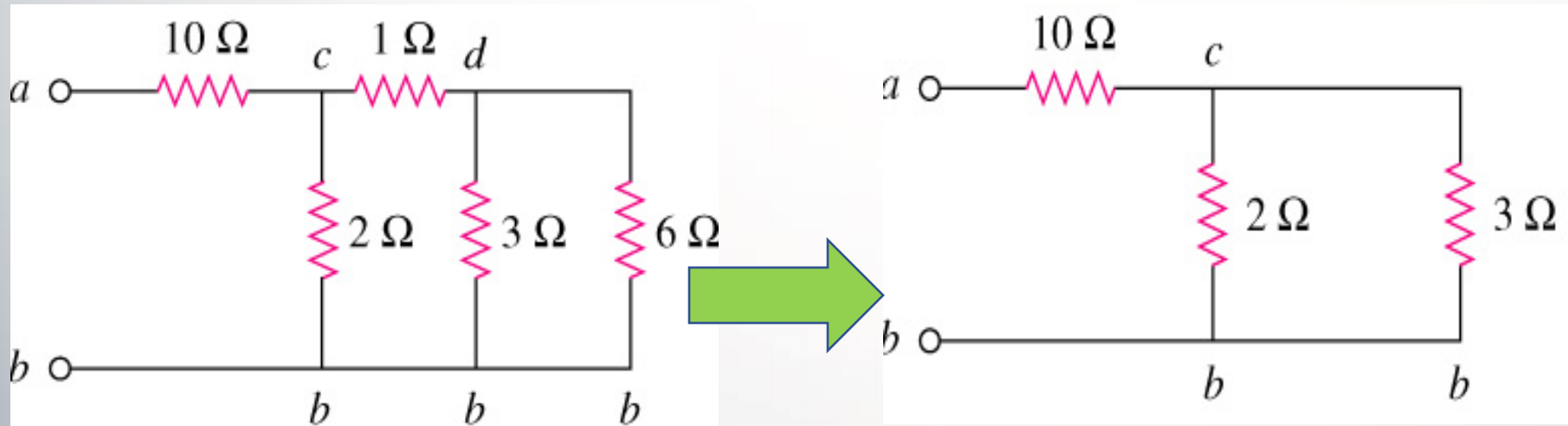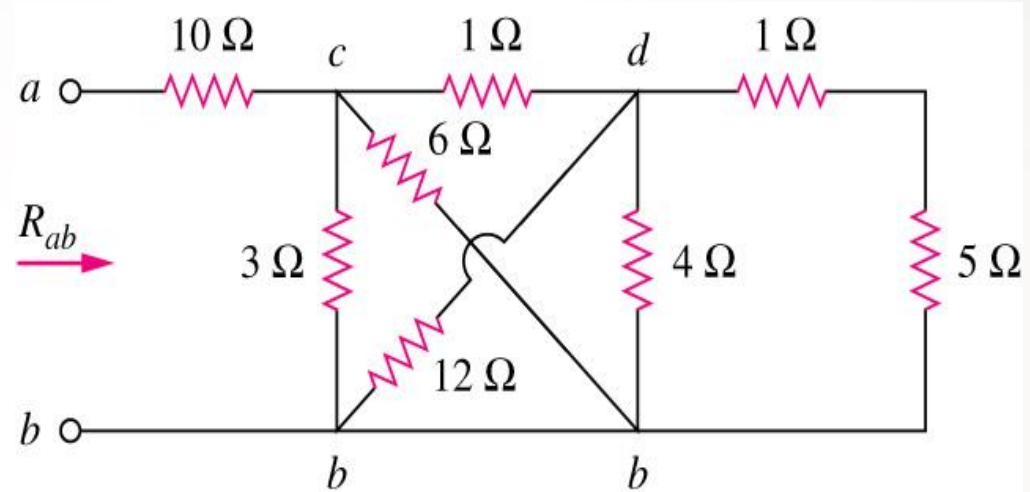


$$R_{eq} = 10 + (3 \times 2) / (3 + 2) = 11.2\ \Omega$$



## Example(12)

Find  $R_{eq}$  for the shown resistor arrangement

**Solution**


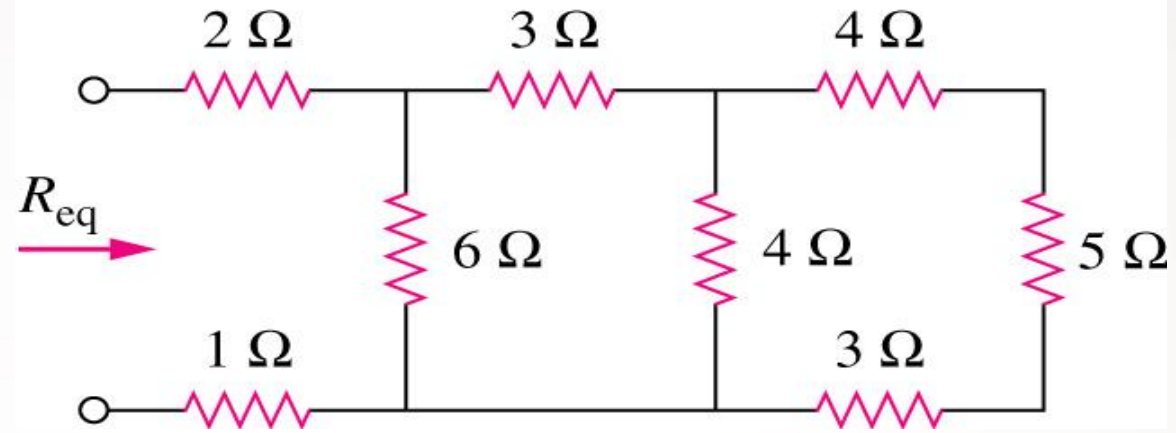


Try to solve

Final answer  $6\ \Omega$
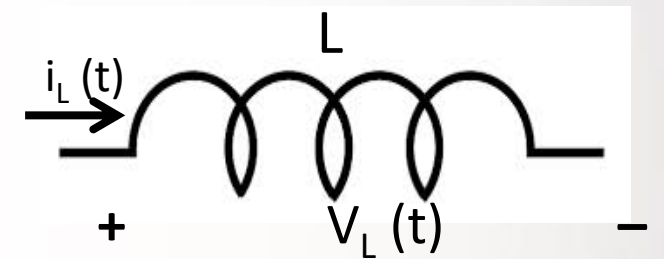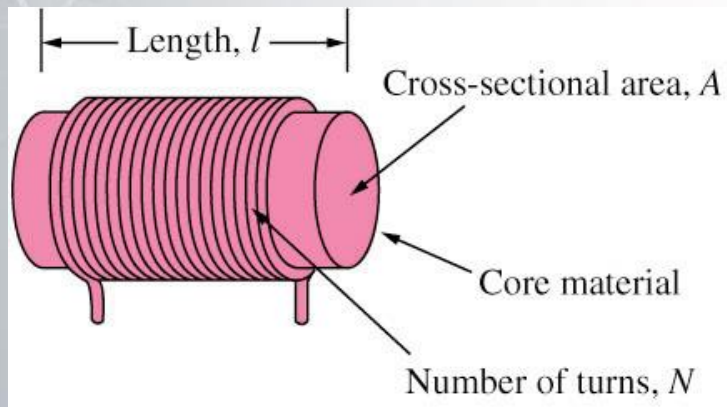
# Inductors

An inductor is a two terminal passive element designed to store energy in its magnetic field.




Follow passive sign convention

An inductor consists of a coil of conducting wire.


- Inductors store electromagnetic energy.
- They may supply stored energy back to the circuit, but they cannot create energy.
- They must abide by the passive sign convention

# Current voltage relationship of an inductor

- The inductor voltage is proportional to the derivative of the current passing through it.
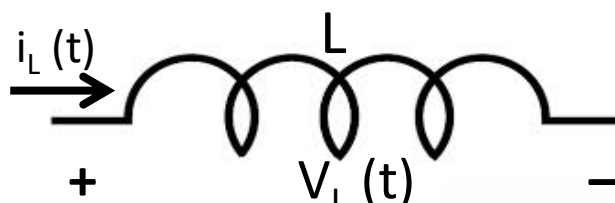
$$v_L(t) = L \frac{di_L(t)}{dt}$$


Where  $L$  is the inductance of the inductor and its unit is Henry (H).
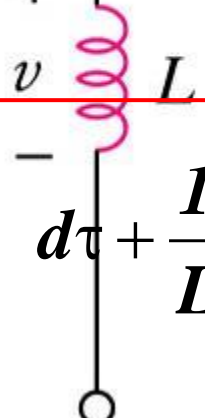
$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(\tau) d\tau = \frac{1}{L} \int_{-\infty}^{t_0} v_L(\tau) d\tau + \frac{1}{L} \int_{t_0}^t v_L(\tau) d\tau$$


- An inductor acts like a short circuit in a DC circuit since  $di/dt = 0$ .
- The inductor current cannot change abruptly.

## Example 7.1 (page 274)

*Find the voltage across the Inductor.*


$$i_L(t) = e^{-t^2}$$

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$v_L(t) = (0.5) \frac{d(e^{-t^2})}{dt}$$

$$v_L(t) = (0.5)(-2t)e^{-t^2}$$

$$v_L(t) = -te^{-t^2} \text{ V}$$

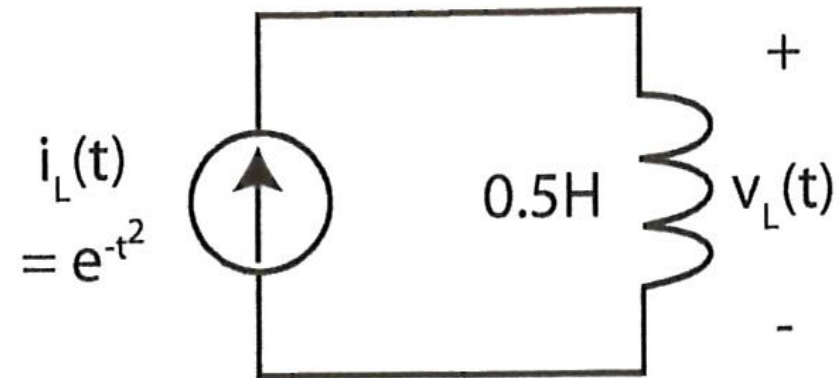

# Series and parallel inductors

The equivalent inductance of **series-connected inductors** is the sum of the individual inductances.

$$v = v_1 + v_2 + v_3 + \dots + v_N$$


Substituting  $v_k = L_k \frac{di}{dt}$  results in:

$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + \dots + L_N \frac{di}{dt}$$

$$= (L_1 + L_2 + L_3 + \dots + L_N) \frac{di}{dt}$$

$$= \left( \sum_{k=1}^N L_k \right) \frac{di}{dt} = L_{eq} \frac{di}{dt} \quad \Rightarrow$$
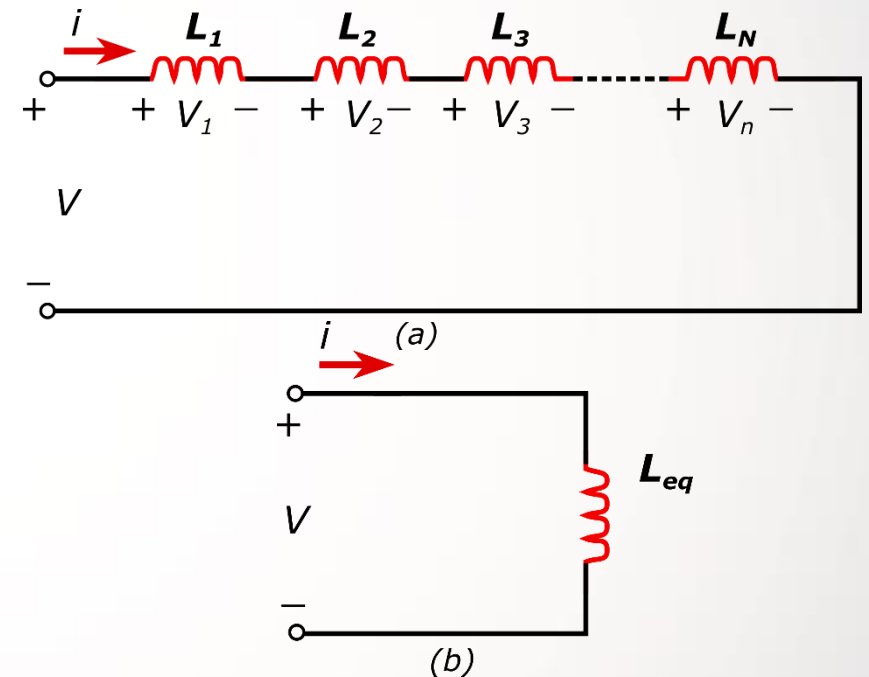
$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$$



# Series and parallel inductors



The equivalent inductance of **parallel inductors** is the reciprocal of the sum of the reciprocals of the individual inductances.

$$i = \frac{1}{L_1} \int_{t_0}^t v dt + i_1(t_0) + \frac{1}{L_2} \int_{t_0}^t v dt + i_2(t_0) + \dots + \frac{1}{L_N} \int_{t_0}^t v dt + i_N(t_0)$$

$$= \left( \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right) \int_{t_0}^t v dt + i_1(t_0) + i_2(t_0) + \dots + i_N(t_0)$$


$$= \left( \sum_{k=1}^N \frac{1}{L_k} \right) \int_{t_0}^t v dt + \sum_{k=1}^N i_k(t_0) = \frac{1}{L_{eq}} \int_{t_0}^t v dt + i(t_0)$$
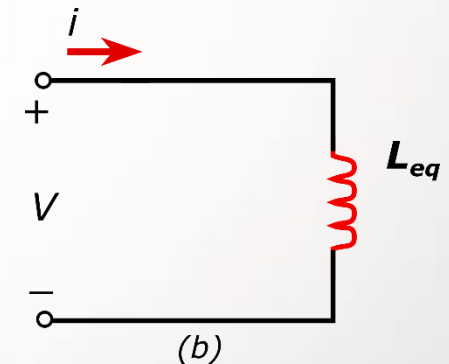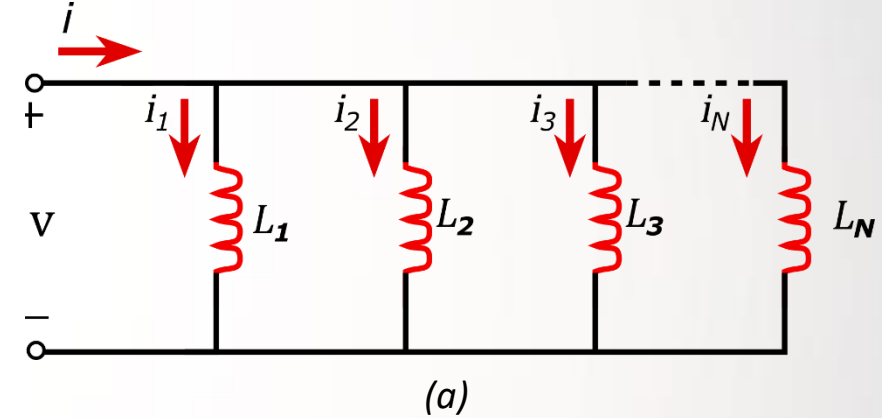
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}$$



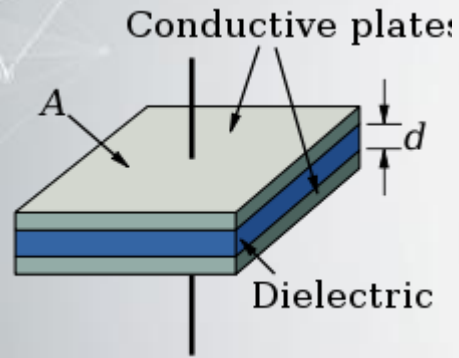
# Capacitors

A capacitor is a passive element designed to store energy in its electric field. It consists of two conducting plates separated by an insulator (or dielectric).



## *Fixed capacitors*

Polyester capacitor

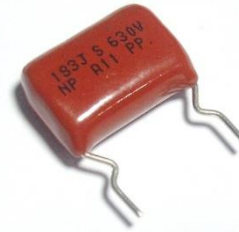

Ceramic capacitor




Electrolytic capacitor



Capacitance of a capacitor is the ratio of the charge on one plate to the voltage difference between the two plates, measured in farads (F).

$$C = q / v$$


**NOTE: 1 farad = 1 coulomb/volt.**

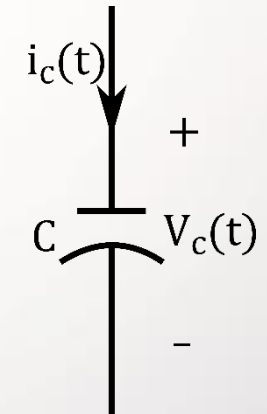


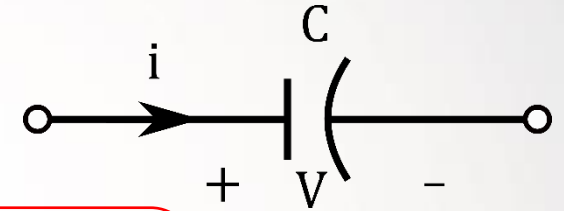
# The current-voltage relationship of a capacitor

- The charge, voltage and capacitance can be mathematically presented as:  $q = C v$



$$\frac{dq}{dt} = C \frac{dv}{dt} \Rightarrow \text{The current in the capacitors is: } i_c = C \frac{dv}{dt}$$

where  $C$  is the capacitance of the capacitor measured in farad (F)

$$v_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(\tau) d\tau = \frac{1}{C} \int_{-\infty}^{t_0} i_c(\tau) d\tau + \frac{1}{C} \int_{t_0}^t i_c(\tau) d\tau$$



$$v_c(t) = v_c(t_0) + \frac{1}{C} \int_{t_0}^t i_c(\tau) d\tau$$

## NOTE

If a DC voltage is applied, the capacitor will be an **open circuit**.

The capacitor voltage **cannot change abruptly**.

allowable  
voltage  
change

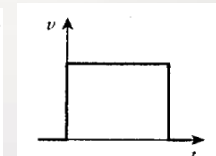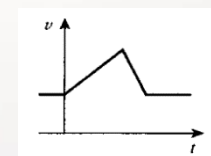

Not  
allowable  
voltage  
change




**Example**

Find the voltage across a capacitor of 2 micro Farads holding 100 micro Coulomb of charge.

$$C = q / v$$
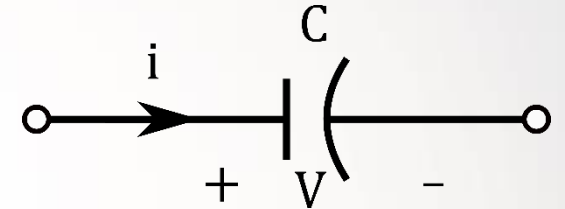
$$v = q / C = \frac{100 \times 10^{-6}}{2 \times 10^{-6}} = 50V$$



**Example**

Determine the voltage across a  $2 \mu\text{F}$  capacitor if the current passing through it is:  **$i(t) = 6e^{-3000t} \text{ mA}$** . Assume  $v(0) = 0$ .

$$v_c(t) = v_c(t_o) + \frac{1}{C} \int_{t_o}^t i_c(\tau) d\tau$$
$$v_c(t) = 0 + \frac{1}{2 \times 10^{-6}} \int_0^t (6 \times 10^{-3}) e^{-3000t} dt$$

$$v_c(t) = 0 + \frac{6 \times 10^{-3}}{-3000 \times 2 \times 10^{-6}} e^{-3000t} \Big|_0^t = (1 - e^{-3000t})V$$

# Series and parallel capacitors



The equivalent capacitance of  $N$  parallel-connected capacitors is the sum of the individual capacitances.

$$i = i_1 + i_2 + i_3 + \cdots + i_N$$

Since  $i_k = C_k \frac{dv}{dt}$ :

$$\begin{aligned} i &= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \cdots + C_N \frac{dv}{dt} \\ &= \left( \sum_{k=1}^N C_k \right) \frac{dv}{dt} = C_{eq} \frac{dv}{dt} \end{aligned}$$
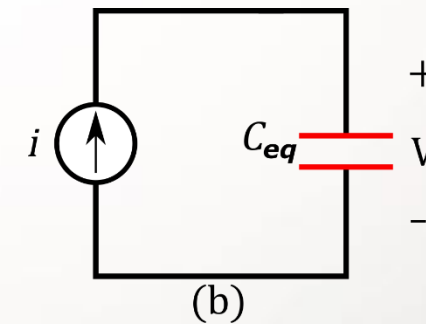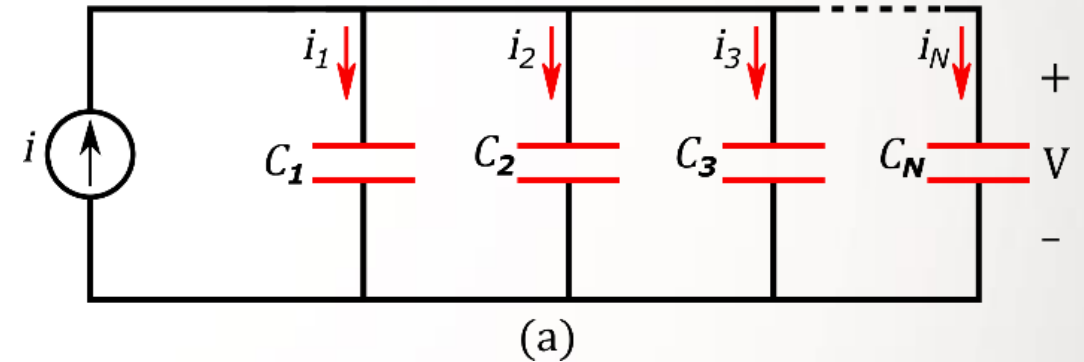
$$C_{eq} = \sum_{k=1}^N C_k = C_1 + C_2 + C_3 + \cdots + C_N$$



# Series and parallel capacitors

The equivalent capacitance of  $N$  series-connected capacitors is the inverse of the sum of the inverses of the individual capacitances.

$$v = v_1 + v_2 + v_3 + \dots + v_N$$


Since  $v_k = \frac{1}{C_k} \int_{t_0}^t i(t) dt + v_k(t_0)$ :

$$v = \frac{1}{C_1} \int_{t_0}^t i(t) dt + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i(t) dt + v_2(t_0) + \dots + \frac{1}{C_N} \int_{t_0}^t i(t) dt + v_N(t_0)$$


$$= \left( \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_{t_0}^t i(t) dt + v_1(t_0) + v_2(t_0) + \dots + v_N(t_0)$$

$$= \frac{1}{C_{eq}} \int_{t_0}^t i(t) dt + v(t_0)$$
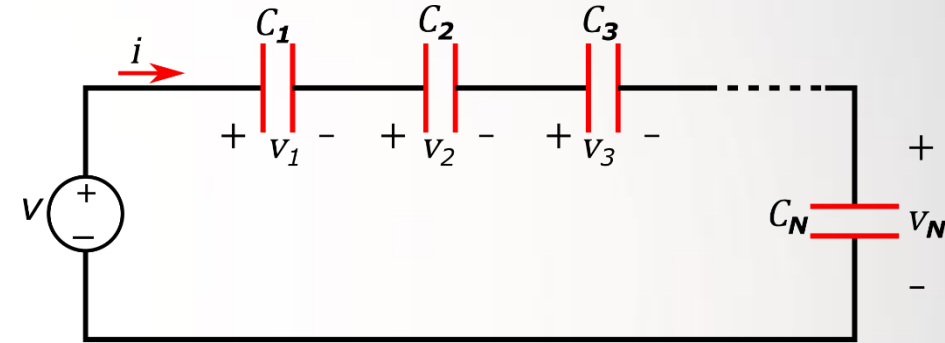
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$




(a)

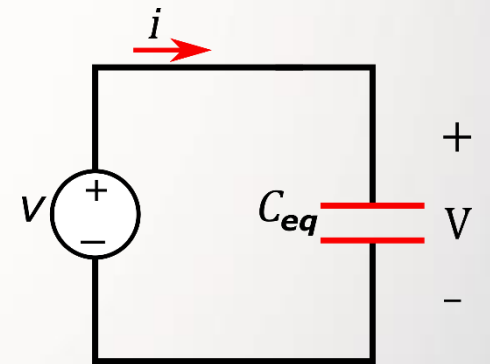

(b)
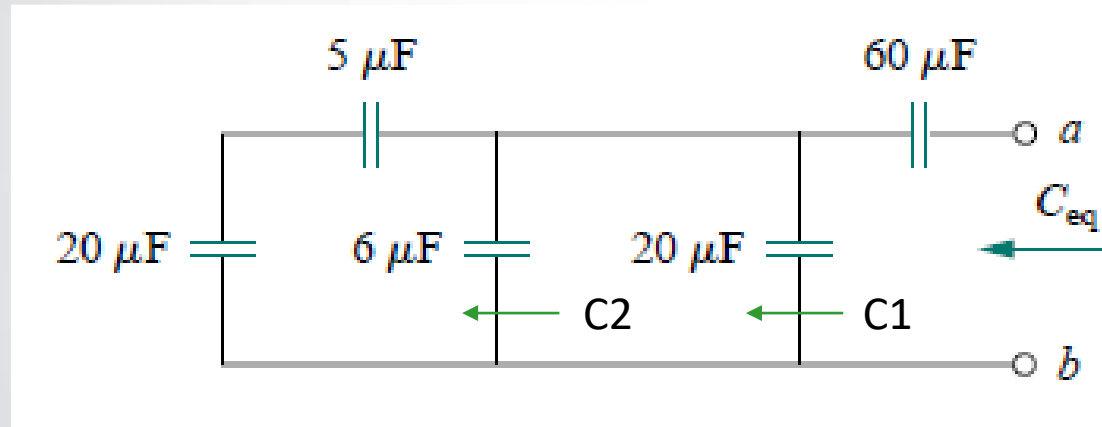
# Example

Find the equivalent capacitance seen between terminals a and b



$$C2 = (20 \times 5 / 25) + 6 = 10\ \mu\text{F}$$

$$C1 = C2 + 10 = 30\ \mu\text{F}$$

$$C_{eq} = \frac{30 \times 60}{30 + 60} = 20\ \mu\text{F}$$