

# Filters – Part B

## Linear Circuit Analysis II EECE 202



# Announcement

1. Midterm during week 8
2. PD 1 Voice Over PPT due in Week 10

# Recap



1. Filters
2. Filter Type
3. Transfer function of a filter
4. Cutoff frequency

## New Material

1. Transfer function of LP, BP, and HP filter

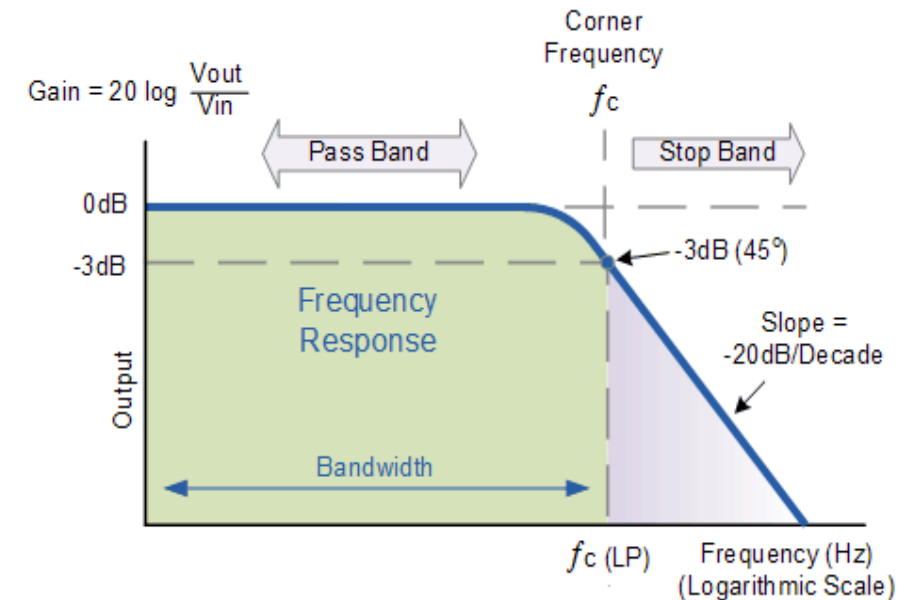
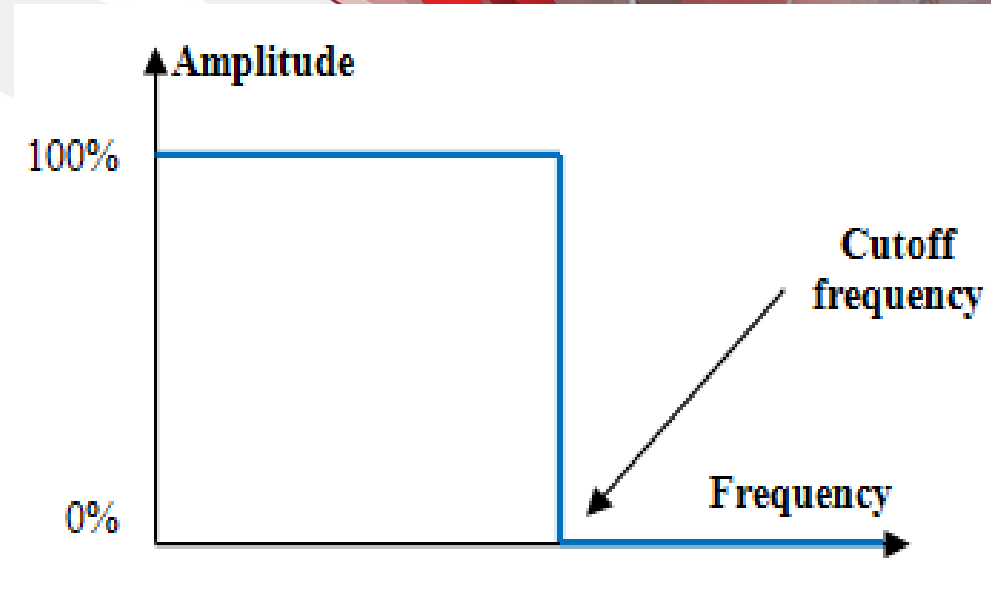
# Low Pass Filter

- The Low pass filter passes signals with frequencies below a certain value ( $f_c$ ), and blocks frequencies above this value. This value ( $f_c$ ) as shown in the figure (shows ideal filter) is called the cutoff frequency.
- The characteristic shown in the figure represents the real response of the low pass filter, where the signal at the cutoff frequency ( $f_c$ ) is attenuated to 70.7% (-3 dB) of its original amplitude.
- The frequencies below this  $f_c$  is called “Pass Band”, and the frequencies above the  $f_c$  is called the “Stop Band”.


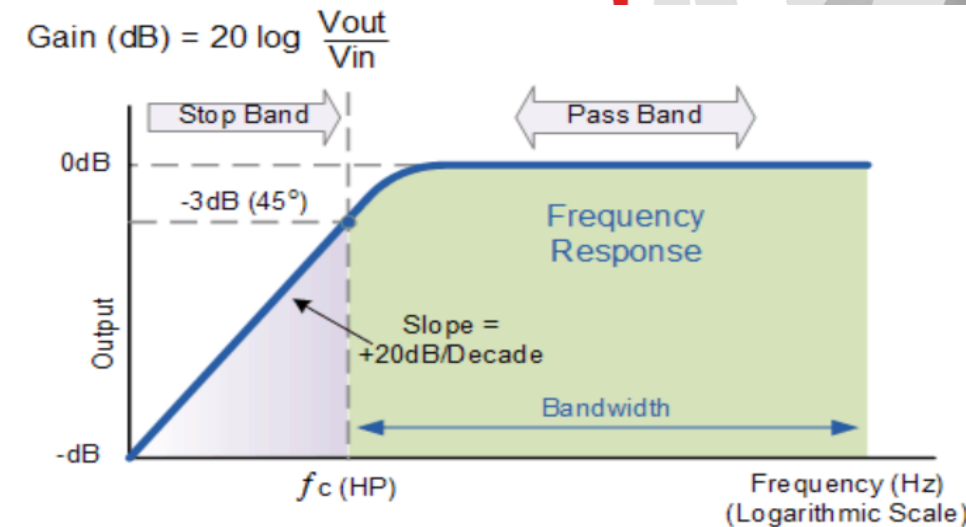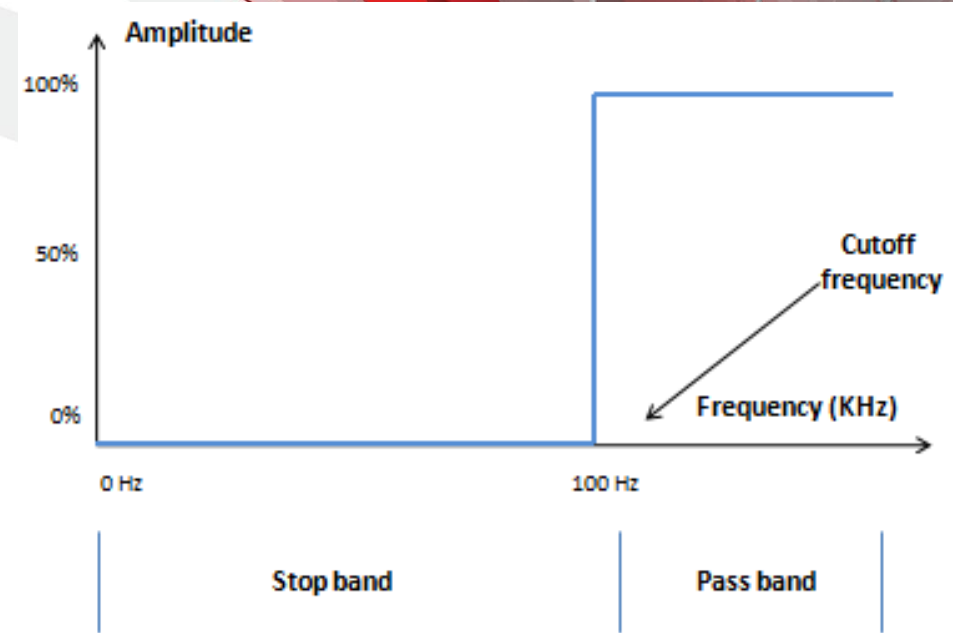
# High pass filter



- The High pass filter passes signals with frequencies above a certain value ( $f_c$ ), and blocks frequencies below this value. This value ( $f_c$ ) as shown in the figure (shows ideal filter) is called the cutoff frequency.
- The characteristic shown in the figure represents the real response of the high pass filter, where the signal at the cutoff frequency ( $f_c$ ) is attenuated to 70.7% (-3 dB) of its original amplitude.
- The frequencies above this  $f_c$  is called “Pass Band”, and the frequencies below the  $f_c$  is called the “Stop Band”.




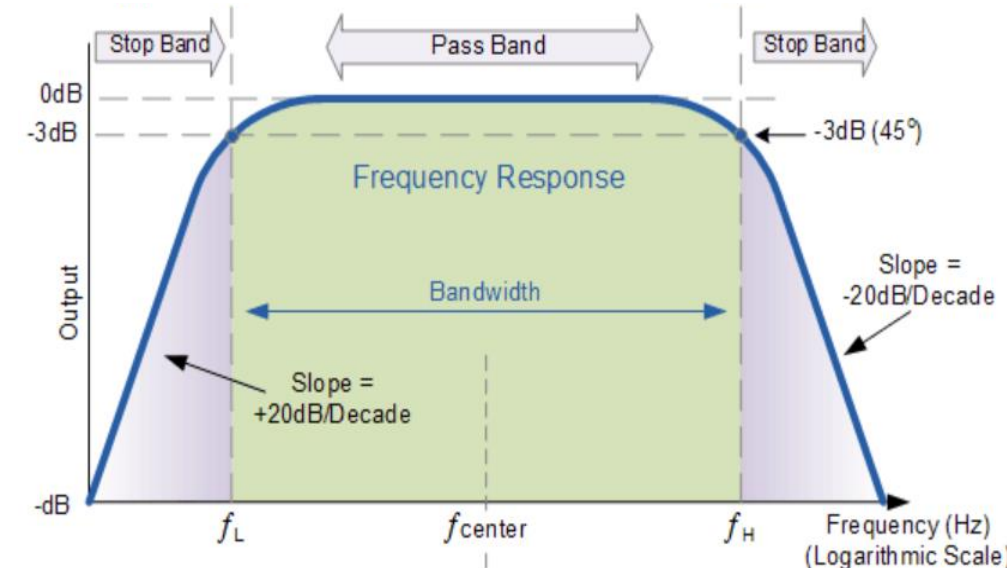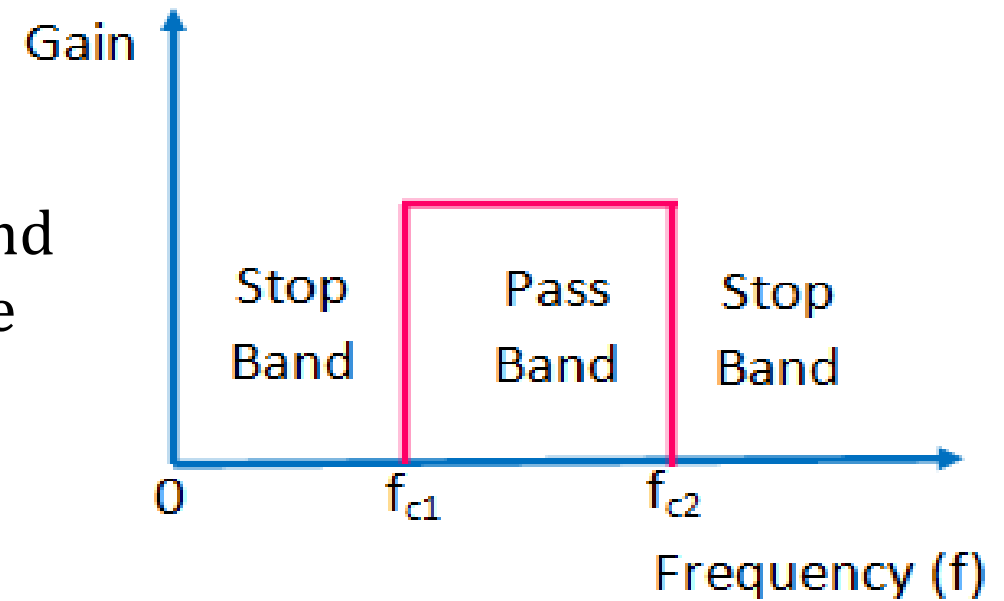
# Bandpass Filter

- The Band pass filter passes signals with frequencies between certain values ( $f_{c1}$ ,  $f_{c2}$ ), and blocks frequencies outside these values. These values ( $f_{c1}$ ,  $f_{c2}$ ) as shown in the figure (shows ideal filter) is called the cutoff frequencies.
- The characteristic shown in the figure represents the real response of the band pass filter, where the signal at the cutoff frequency ( $f_{c1}$  and  $f_{c2}$ ) are attenuated to 70.7% (-3 dB) of its original amplitude.
- The frequencies in between these  $f_{c1}$  and  $f_{c2}$  are called “Pass Band”, and the frequencies outside the  $f_{c1}$  and  $f_{c2}$  are called the “Stop Band”.



# High Pass Filter (HPF)

The opposite of the low-pass is the high-pass filter, which rejects signals below its cutoff frequency.

$$H(S) = \frac{KS^2}{S^2 + 2\sigma S + \omega_o^2}$$

The poles of the TF are :  $P_{1,2} = -\sigma \pm j\omega_d$

$\omega_o$ : is the magnitude of pole frequency like in BP filter, and  $\sigma$  is the real part of the pole frequency


The peak frequency is :  $\omega_o = \sqrt{\sigma^2 + \omega_d^2}$

The gain (amplitude) of the frequency response is given by:

$$\begin{aligned} |H(j\omega)| &= \left| \frac{-K\omega^2}{-\omega^2 + 2\sigma j\omega + \omega_0^2} \right| = \frac{K\omega^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\sigma^2\omega^2}} \\ &= \frac{K\left(\frac{\omega}{\omega_0}\right)^2}{\sqrt{\left(1 - \frac{\omega^2}{\omega_0^2}\right)^2 + 4\left(\frac{\sigma\omega}{\omega_0^2}\right)^2}} \end{aligned}$$

The phase response is given by:

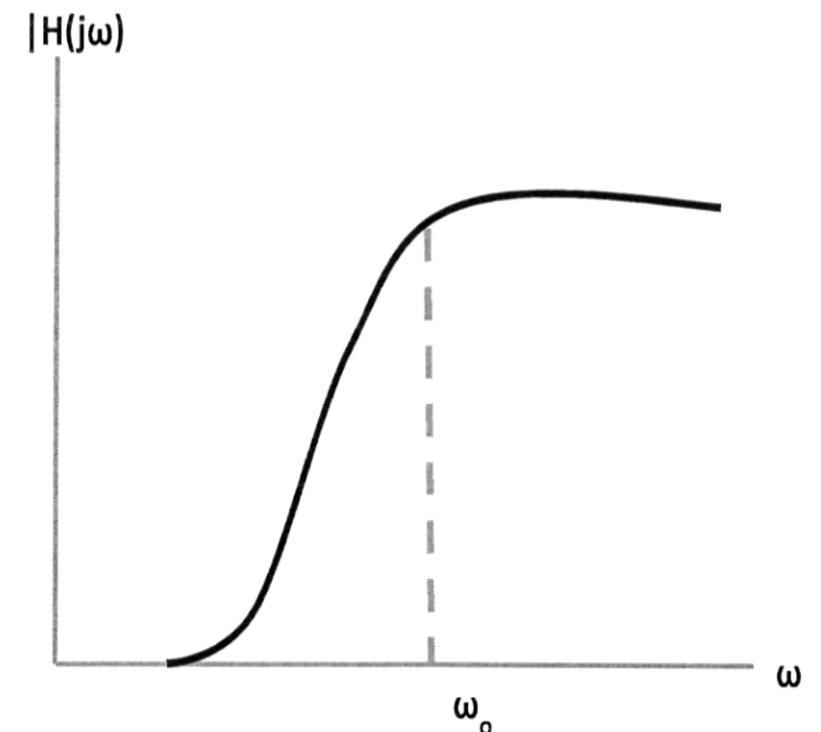
$$\theta(\omega) = \arg H(s) = 180 - \tan^{-1} \left[ \frac{2\sigma\omega}{(\omega_0^2 - \omega^2)} \right]$$




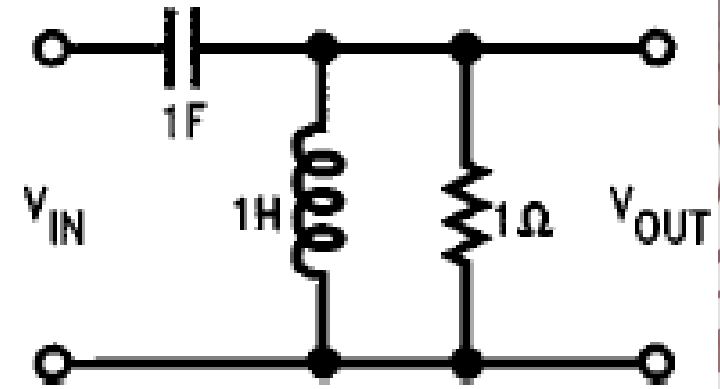
# Example

- 1- Find the transfer function of the shown circuit.
- 2- What kind of filter does this circuit represent.
- 3- Find the peak frequency ( $\omega_0$ ) and the gain factor "K".



Consider  $Z_{in} = \frac{1}{sC} = \frac{1}{s}$ , and  $Z_{out} = sL || 1 = s || 1 = \frac{s}{s+1}$

Then the TF will be:  $\frac{V_{out}}{V_{in}} = \frac{Z_{out}}{Z_{in} + Z_{out}} = \frac{\frac{s}{s+1}}{\frac{1}{s} + \frac{s}{s+1}} = \frac{\frac{s}{s+1}}{\frac{s+1}{s(s+1)} + \frac{s \times s}{s(s+1)}} = \frac{\frac{s}{s+1}}{\frac{s^2 + s + 1}{s(s+1)}} = \frac{s^2}{s^2 + s + 1}$

There is an " $s^2$ " on the numerator, then this is a **High Pass Filter**.

By matching the below 2 equations, we can easily find  $\omega_0=1$ , and  $K=1$

$$H(S) = \frac{KS^2}{S^2 + 2\sigma S + \omega_0^2} \quad \& \quad \frac{V_{out}}{V_{in}} = \frac{s^2}{s^2 + s + 1}$$

# Band Pass (BP) Filter

The general TF of a 2<sup>nd</sup> order BPF

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{K * S}{s^2 + (\frac{\omega_p}{Q_p})s + \omega_p^2} = \frac{K * S}{s^2 + 2\sigma s + \omega_p^2}$$


The poles of the TF are :  $P_{1,2} = -\sigma \pm j\omega_d$

The peak frequency is :  $\omega_p = \sqrt{\sigma^2 + \omega_d^2}$

The Bandwidth is :  $B_\omega = \frac{\omega_p}{Q_p} = 2\sigma = \omega_2 - \omega_1$

The maximum value:  $H_m = \frac{K}{2\sigma} = \frac{K}{B_\omega} = \frac{K * Q_p}{\omega_p}$

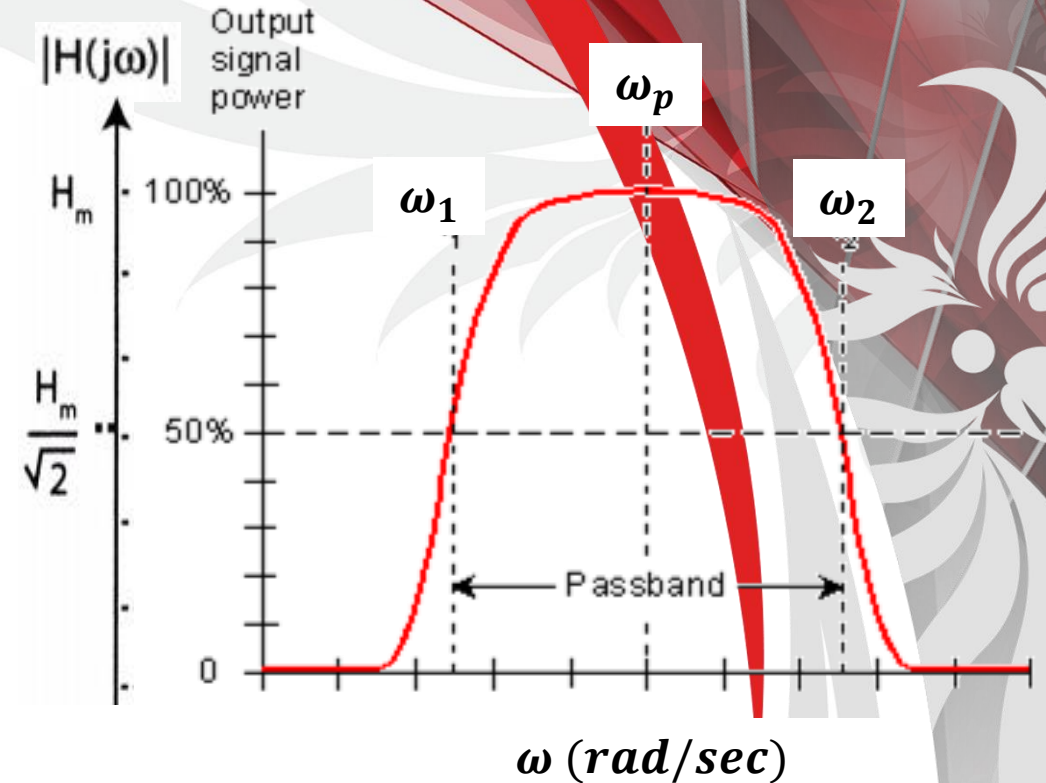The Quality factor:  $Q_p = \frac{\omega_p}{B_\omega}$



$$\omega_{1,2} = \omega_p \left( \sqrt{1 + \frac{1}{4Q_p^2}} \pm \frac{1}{2Q_p} \right)$$

# Example -1

For the circuit shown, answer the following:


1-Find the transfer function  $H(s)$ .

2-What kind of filter does this circuit represent.

3-Find the magnitude and the phase of the transfer function as a function of " $\omega$ ".

Solution
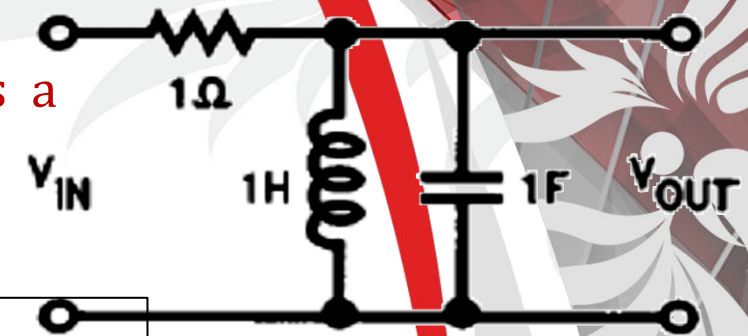
$$H(s) = \frac{\frac{s \times \frac{1}{s}}{s + \frac{1}{s}}}{1 + \frac{s \times \frac{1}{s}}{s + \frac{1}{s}}} = \frac{\frac{1}{\frac{s^2 + 1}{s}}}{1 + \frac{1}{\frac{s^2 + 1}{s}}} = \frac{\frac{s}{s^2 + 1}}{1 + \frac{s}{s^2 + 1}} = \frac{\frac{s}{s^2 + 1}}{\frac{s^2 + 1 + s}{s^2 + 1}} = \frac{s}{s^2 + s + 1}$$



$H(s)$  is like  $\frac{K*s}{s^2+2\sigma s+\omega_p^2}$   
so the circuit represents a  
band pass filter

$$A(\omega) = |H(s)| = \left| \frac{j\omega}{-\omega^2 + j\omega + 1} \right|$$
$$= \frac{\omega}{\sqrt{\omega^2 + (1 - \omega^2)^2}}$$
$$\theta(\omega) = \arg H(s) = 90^\circ - \tan^{-1} \frac{\omega^2}{(1 - \omega^2)}$$

## Example -2

Suppose a second-order BP-filter circuit having the transfer function:

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{2S}{S^2 + 2S + 256}$$

Find  $H_m, \omega_p, B_w$  and  $\omega_{1,2}$ . Also, draw the response and indicate the obtained values.

$$\begin{aligned} H(s) &= \frac{K \cdot S}{S^2 + 2\sigma S + \omega_p^2} \\ &= \frac{K \cdot S}{S^2 + \frac{\omega_p}{Q_p} S + \omega_p^2} \end{aligned}$$

$$\begin{aligned} K &= 2, \\ \omega_p &= \sqrt{256} = 16 \frac{\text{rad}}{\text{s}}, \\ B_w &= 2\sigma = 2 \text{ rad/s}, \\ Q_p &= \frac{\omega_p}{2\sigma} = \frac{16}{2} = 8, \end{aligned}$$

$$\begin{aligned} \omega_1 &= 16 \sqrt{1 + \frac{1}{4 \times 64} - \frac{1}{2 \times 8}} = 15 \text{ rad/s} \\ \omega_2 &= 16 \sqrt{1 + \frac{1}{4 \times 64} + \frac{1}{2 \times 8}} = 17 \text{ rad/s} \end{aligned}$$

$\omega_p = 16 \text{ rad/sec}$ ,  $B_w = 2 \text{ rad/sec}$ ,  $H_m = 1$ ,  $\omega_1 = 15 \text{ rad/sec}$  and  $\omega_2 = 17 \text{ rad/sec}$ .



## Example -3


For the shown circuit, find the transfer function

$$\frac{V_{out}(s)}{I_{in}(s)} = Z_{in}(s) .$$

Use  $R=2.5K \Omega$ ,  $L=0.1H$ ,  $C=0.1\mu F$

Also, find  $H_m$ ,  $\omega_p$ ,  $B_w$  and  $\omega_{1,2}$ .

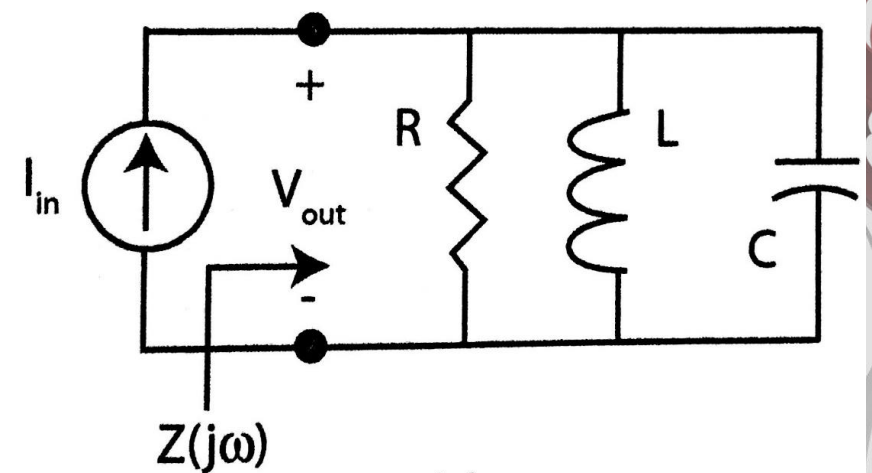Draw the response and indicate the obtained values.



## Example -3

$$\frac{V_{out}(s)}{I_{in}(s)} = Z(s) = \frac{1}{Y(s)} = \frac{1}{Cs + \frac{1}{R} + \frac{1}{Ls}} = \frac{1}{\frac{RLCs^2 + Ls + R}{RLs}} = \frac{RLs}{RLCs^2 + Ls + R}$$

$$\rightarrow Z(s) = \frac{RLs}{RLCs^2 + Ls + R} = \frac{\frac{RLs}{RLC}}{\frac{RLCs^2}{RLC} + \frac{Ls}{RLC} + \frac{R}{RLC}} = \frac{\frac{1}{C}s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

Compare this equation:

$$\frac{\frac{1}{C}s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

With the BPF equation:

$$\frac{Ks}{s^2 + 2\sigma s + \omega_p^2}$$

## Example 3

$$\frac{\frac{1}{C}s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

$$\frac{Ks}{s^2 + 2\sigma s + \omega_p^2}$$

$$\left. \begin{aligned} \sigma &= \frac{1}{2RC} \\ \omega_p &= \frac{1}{\sqrt{LC}} \end{aligned} \right\}$$

$$Q_p = \frac{\omega_p}{2\sigma} = \frac{RC}{\sqrt{LC}} = R \sqrt{\frac{L}{C}}$$

$$\omega_p = \frac{1}{\sqrt{LC}}$$

$$K = \frac{1}{C}$$

$$H_m = \frac{K}{2\sigma} = \frac{1/C}{1/RC} = R$$

Now, replace each parameter with its value in the example.

$$\omega_{1,2} = \frac{1}{\sqrt{LC}} \left( \sqrt{1 + \frac{1}{4R^2 \frac{C}{L}}} \mp \frac{1}{2R \sqrt{\frac{C}{L}}} \right) = \frac{1}{\sqrt{LC}} \left( \sqrt{\frac{4R^2 C + L}{4R^2 C}} \mp \frac{1}{2R \sqrt{\frac{C}{L}}} \right)$$

$$= \left( \sqrt{\frac{4R^2 C + L}{4R^2 LC^2}} \mp \frac{1}{2R \sqrt{LC \frac{C}{L}}} \right) = \sqrt{\frac{1}{LC} + \left(\frac{1}{2RC}\right)^2} \mp \frac{1}{2RC}$$

# Answer the following questions using ChatGPT

- How do filters affect the amplitude of signals within their pass band and stop band.
- Give an example where each filter type might be practically applied in electronic or communication systems
- Which property of a filter describes its ability to distinguish between closely spaced frequencies.
- Which filter blocks only a specific narrow band of frequencies while passing all others.



# Summary

- Low-Pass Filter (LPF) allows frequencies below the cutoff frequency ( $f_c$ ) to pass and attenuates frequencies above  $f_c$ . Used to remove high-frequency noise from signals.
- High-Pass Filter (HPF) allows frequencies above the cutoff frequency ( $f_c$ ) to pass, attenuates frequencies below  $f_c$ , useful in applications that require eliminating low-frequency noise or interference.
- Band-Pass Filter (BPF) passes frequencies within a specific range ( $f_{c1}$  to  $f_{c2}$ ), attenuates frequencies outside this range, and ideal for isolating specific frequency bands.
- Notch (Band-Stop) Filter attenuates a narrow band of frequencies, passes frequencies outside this band, used to eliminate unwanted frequencies.
- Key Concepts
  - At cutoff frequency signal amplitude drops to 70.7% (-3 dB).
  - Pass Band & Stop Band: Frequency ranges that are passed or attenuated by the filter.
  - Quality Factor (Q) indicates the filter's selectivity and ability to distinguish between frequencies.